


Lecture 11: Sequential Circuit Design

Outline

- ☐ Sequencing
- ☐ Sequencing Element Design
- ☐ Max and Min-Delay
- ☐ Clock Skew
- ☐ Time Borrowing
- ☐ Two-Phase Clocking

Sequencing

 - ❑ *Combinational logic*
 - output depends on current inputs
- ❑ *Sequential logic*
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



11: Sequential Circuits

CMOS VLSI Design 4th Ed.

3

Sequencing Cont.

- ❑ If tokens moved through pipeline at constant speed, no sequencing elements would be necessary
- ❑ Ex: fiber-optic cable
 - Light pulses (tokens) are sent down cable
 - Next pulse sent before first reaches end of cable
 - No need for hardware to separate pulses
 - But *dispersion* sets min time between pulses
- ❑ This is called *wave pipelining* in circuits
- ❑ In most circuits, dispersion is high
 - Delay fast tokens so they don't catch slow ones

11: Sequential Circuits

CMOS VLSI Design 4th Ed.


4

Sequencing Overhead

- ❑ Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.
- ❑ Inevitably adds some delay to the slow tokens
- ❑ Makes circuit slower than just the logic delay
 - Called sequencing overhead
- ❑ Some people call this clocking overhead
 - But it applies to asynchronous circuits too
 - Inevitable side effect of maintaining sequence

Sequencing Elements

 - ❑ **Latch:** Level sensitive
 - a.k.a. transparent latch, D latch
- ❑ **Flip-flop:** edge triggered
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- ❑ Timing Diagrams
 - Transparent
 - Opaque
 - Edge-trigger



Latch Design

☐ Pass Transistor Latch

☐ Pros

+

+

☐ Cons

-


-

-

-

-

-

 


Used in 1970's

Latch Design

☐ Transmission gate

+

-

 

Latch Design

☐ Inverting buffer

+


+

+ Fixes either

•

•

—

 


Latch Design

☐ Tristate feedback

+

—

 
☐ Static latches are now essential because of leakage



Latch Design

□ Buffered input


+
+

 

Latch Design

□ Buffered output

+

 


□ Widely used in standard cells

- + Very robust (most important)
- Rather large
- Rather slow (1.5 – 2 FO4 delays)
- High clock loading

Latch Design



□ Datapath latch

+
+
-

 


Flip-Flop Design

  □ Flip-flop is built as pair of back-to-back latches



Enable

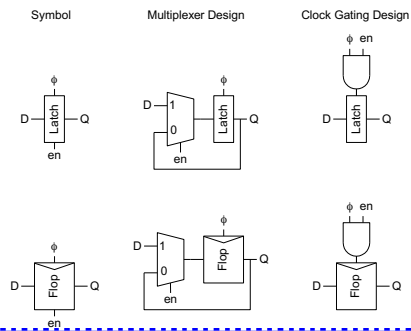- ❑ Enable: ignore clock when en = 0
 - Mux: increase latch D-Q delay
 - Clock Gating: increase en setup time, skew




11: Sequential Circuits

CMOS VLSI Design 4th Ed.

15

Reset

 - ❑ Force output low when reset asserted
- ❑ Synchronous vs. asynchronous




11: Sequential Circuits

CMOS VLSI Design 4th Ed.

16

Set / Reset

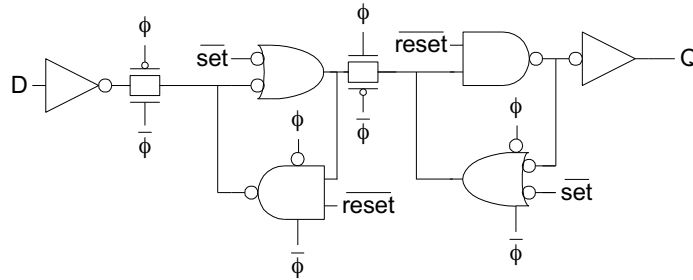- ❑ Set forces output high when enabled
- ❑ Flip-flop with asynchronous set and reset




11: Sequential Circuits

CMOS VLSI Design 4th Ed.

17

Sequencing Methods

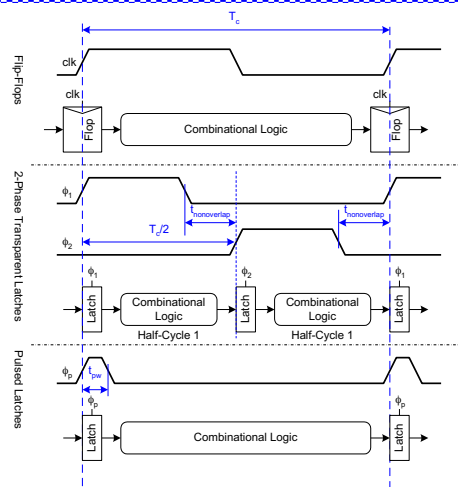- ❑ Flip-flops
- ❑ 2-Phase Latches
- ❑ Pulsed Latches



11: Sequential Circuits


CMOS VLSI Design 4th Ed.

18


Timing Diagrams

Contamination and Propagation Delays


| | |
|-------------|-------------------------------|
| t_{pd} | Logic Prop. Delay |
| t_{cd} | Logic Cont. Delay |
| t_{pcq} | Latch/Flop Clk->Q Prop. Delay |
| t_{ccq} | Latch/Flop Clk->Q Cont. Delay |
| t_{pdq} | Latch D->Q Prop. Delay |
| t_{cdq} | Latch D->Q Cont. Delay |
| t_{setup} | Latch/Flop Setup Time |
| t_{hold} | Latch/Flop Hold Time |

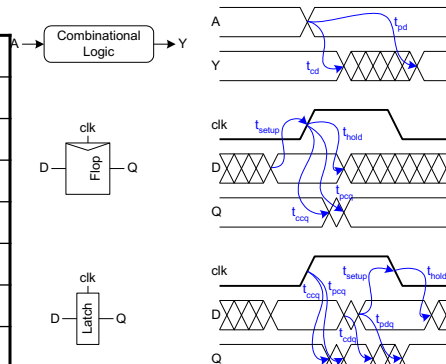

Max-Delay: Flip-Flops

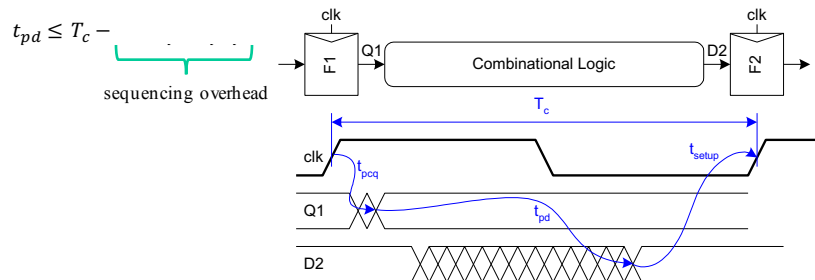

Max Delay: 2-Phase Latches

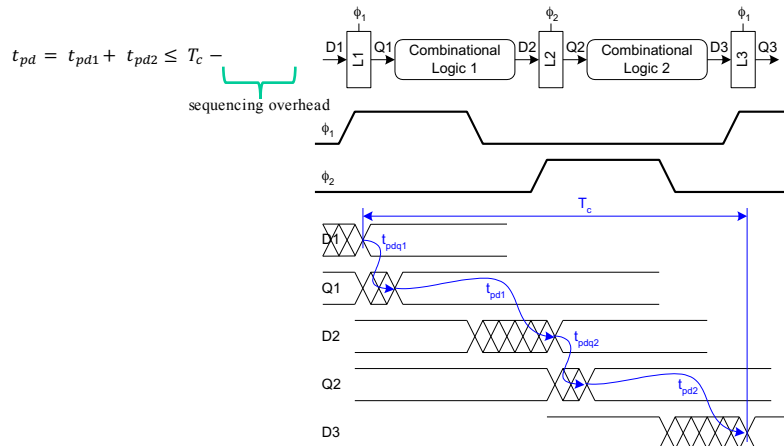


11: Sequential Circuits

CMOS VLSI Design 4th Ed.

21

Max Delay: Pulsed Latches

 


11: Sequential Circuits

CMOS VLSI Design 4th Ed.

22

Min-Delay: Flip-Flops

$$t_{cd} \geq$$

 


Min-Delay: 2-Phase Latches

$$t_{cd1}, t_{cd2} \geq$$

Hold time reduced by nonoverlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

 

Min-Delay: Pulsed Latches

$$t_{cd} \geq$$


Hold time increased
by pulse width

 

Time Borrowing

- ❑ In a flop-based system:
 - Data launches on one rising edge
 - Must setup before next rising edge
 - If it arrives late, system fails
 - If it arrives early, time is wasted
 - Flops have hard edges
- ❑ In a latch-based system
 - Data can pass through latch while transparent
 - Long cycle of logic can borrow time into next
 - As long as each loop completes in one cycle

Time Borrowing Example

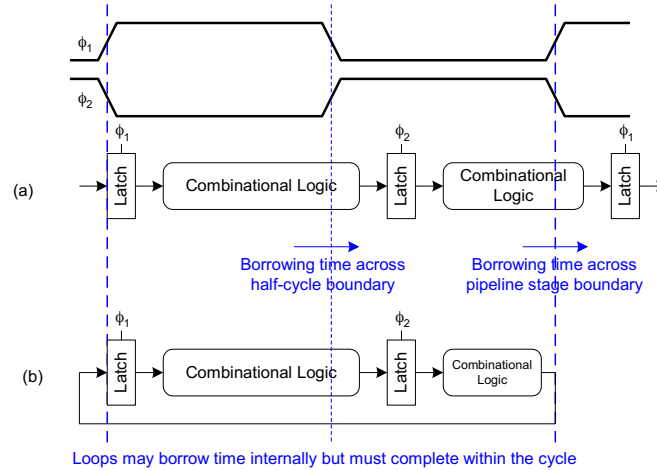


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
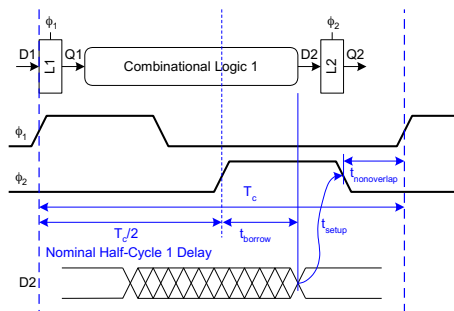
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$




Clock Skew

- ❑ We have assumed zero clock skew
- ❑ Clocks really have uncertainty in arrival time
 - Decreases maximum propagation delay
 - Increases minimum contamination delay
 - Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
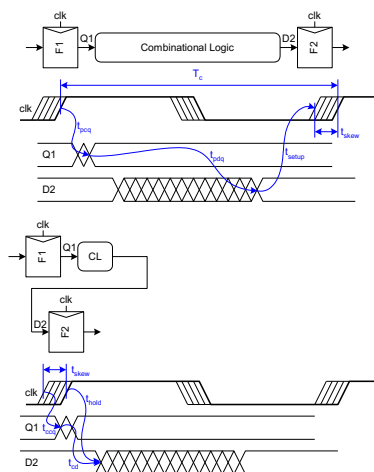
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(t_{setup} + t_{peq})}_{\text{sequencing overhead}}$$

$$t_{cd1}t_{cd2} \geq t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$$
 
$$t_{borrow} \leq \frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{hold} + t_{pw} - t_{ccq} + t_{skew}$$


$$t_{borrow} \leq t_{pw} - (t_{setup} + t_{skew})$$

Two-Phase Clocking

- ☐ If setup times are violated, reduce clock speed
- ☐ If hold times are violated, chip fails at any speed
- ☐ In this class, working chips are most important
 - No tools to analyze clock skew
- ☐ An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- ☐ Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

 - ❑ Past years used flip-flop with nonoverlapping clocks
 - Slow – nonoverlap adds to setup time
 - But no hold times
- ❑ In industry, use a better timing analyzer
 - Add buffers to slow signals if hold time is at risk




11: Sequential Circuits

CMOS VLSI Design 4th Ed.

33

Adaptive Sequencing

 - ❑ Designers include timing margin
 - Voltage
 - Temperature
 - Process variation
 - Data dependency
 - Tool inaccuracies
- ❑ Alternative: run faster and check for near failures
 - Idea introduced as “Razor”
 - Increase frequency until at the verge of error
 - Can reduce cycle time by ~30%



11: Sequential Circuits

CMOS VLSI Design 4th Ed.

34

Summary

- ❑ Flip-Flops:
 - Very easy to use, supported by all tools
- ❑ 2-Phase Transparent Latches:
 - Lots of skew tolerance and time borrowing
- ❑ Pulsed Latches:
 - Fast, some skew tol & borrow, hold time risk

| | Sequencing overhead ($T_c - t_{pd}$) | Minimum logic delay t_{cd} | Time borrowing t_{borrow} |
|-------------------------------------|----------------------------------------------------------------|-----------------------------------------------------------------------|-----------------------------------------------------------|
| Flip-Flops | $t_{pcq} + t_{setup} + t_{skew}$ | $t_{hold} - t_{cq} + t_{skew}$ | 0 |
| Two-Phase Transparent Latches | $2t_{pdq}$ | $t_{hold} - t_{cq} - t_{nonoverlap} + t_{skew}$ in each half-cycle | $\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$ |
| Pulsed Latches | $\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\bar{w}} + t_{skew})$ | $t_{hold} - t_{cq} + t_{p\bar{w}} + t_{skew}$ | $t_{p\bar{w}} - (t_{setup} + t_{skew})$ |