



DREXEL UNIVERSITY

Electrical and Computer Engineering

College of Engineering

Drexel University

Electrical and Computer Engineering Dept.

Electrical Engineering Laboratory IV, ECEL-304

TITLE: Step 3

NAME: Sunny Shah

PARTNER: Derek Philibert

TA: Weston Aenchbacher

SECTION: 62

DATE PERFORMED: 1/19/2017

DATE DUE: 1/27/2017

DATE RECEIVED:

Objective

The objective of this lab was to test the limitation of the ADC0804 and DAC0808 by experimenting with the voltage and time resolutions. The analog voltage was fed into the ADC in CFR or continuous free running mode then reconstructed the analog voltage with the DAC along an 8 bit bus, as shown in figure 1. This experiment will be done at different frequencies to test the limits of the system.

Add DAC to the existing ADC in CFR

 


Figure 1: DAC and ADC system

Results

 


Figure 2: Input vs Output of DAC0808; 1 Hz Ramp input

 


Figure 3: Time Step Measurement of output of DAC0808, 1 Hz Ramp input

 


Figure 4: Time Step Measurement of output of DAC0808, 10Hz Ramp input

 


Figure 5: Time Step Measurement of output of DAC0808, 100 Hz Ramp input

 


Figure 6: Time Step Measurement of output of DAC0808, 1k Hz Ramp input

 


Figure 7: Input vs Output of Multisim Simulation, 1 Hz Ramp input

 


Figure 8: Time Step Measurement of Multisim Simulation, 1 Hz Ramp input

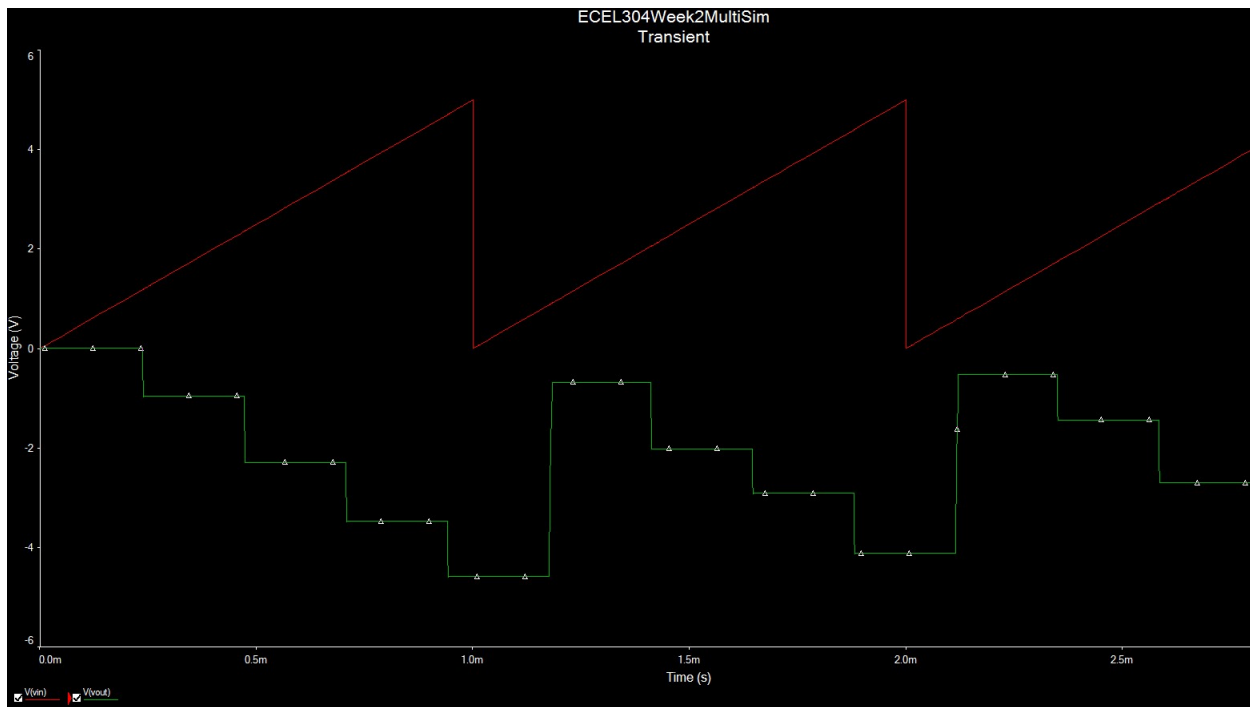


Figure 9: Input vs Output of Multisim Simulation, 1 kHz Ramp Input

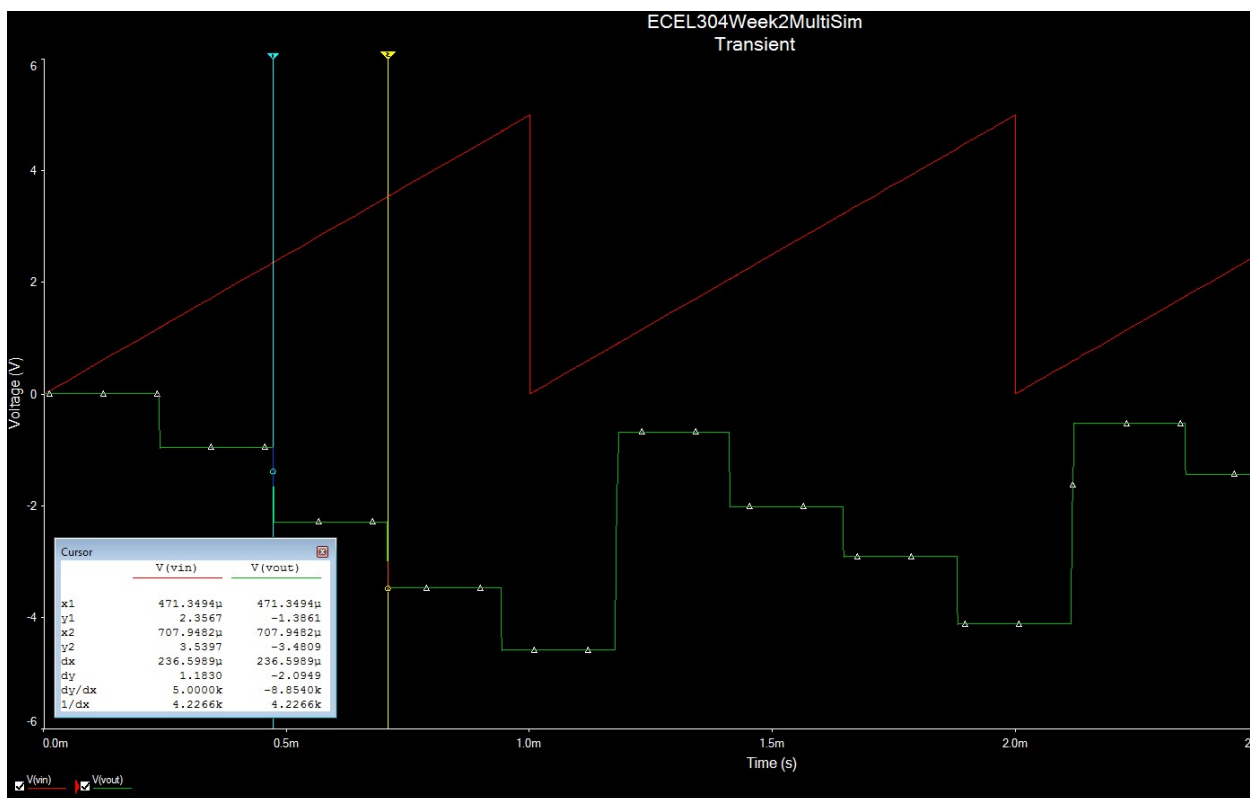


Figure 10: Time Step Measurement of Multisim Simulation, 1 kHz Ramp Input

 


Figure 11: Input vs Output of Multisim Simulation, 10 Hz Ramp input

 


Figure 12: Time Step Measurement of Multisim Simulation, 10 Hz Ramp input

 


Figure 13: Input vs Output of Multisim Simulation, 100 Hz Ramp input

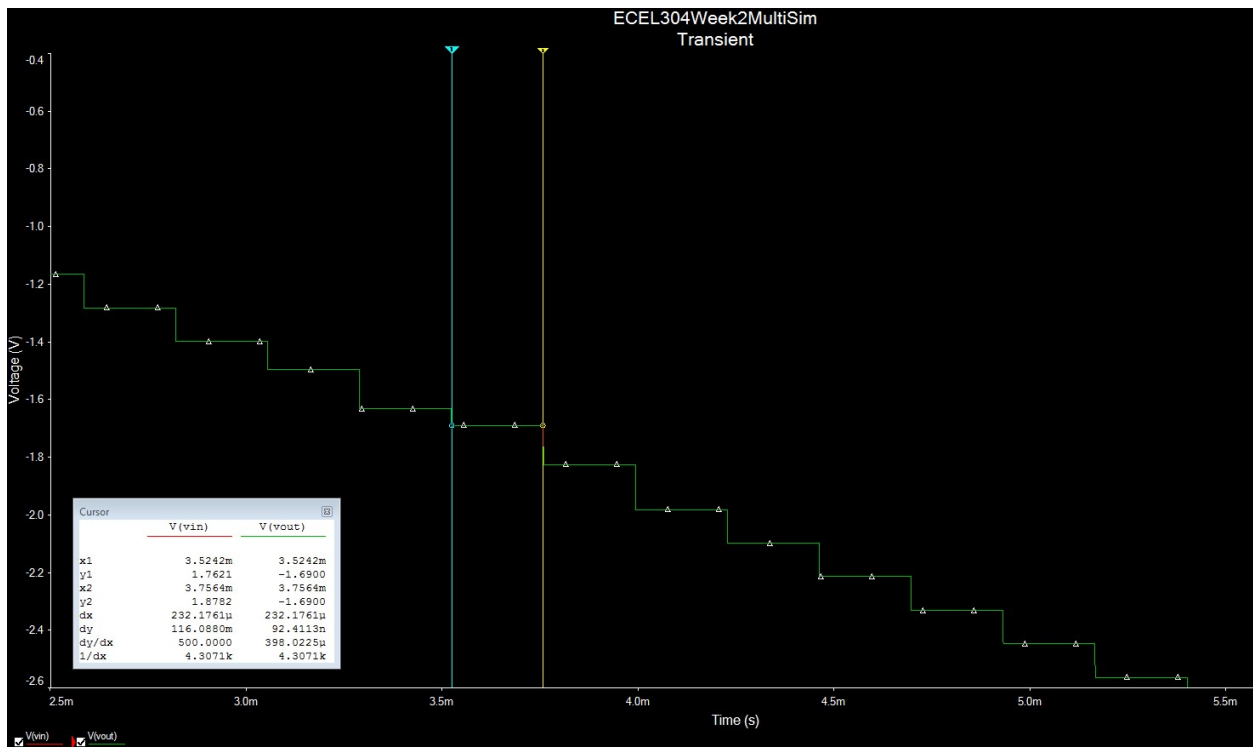


Figure 14: Time Step Measurement of Multisim Simulation, 100 Hz Ramp input

 


Figure 15: Output of DAC0808 aliasing, 1 kHz Sine Wave input

 


Figure 16: Schematic used for simulation in Multisim

Table 1: Comparing Simulation results with Actual Results

| Input Freq (Hz) | Simulated Time Step (s) | Actual Time Step (s) | Time Step Percent Error (%) | Simulated Freq (Hz) | Actual Freq (Hz) | Freq Percent Error (%) |
|-----------------|-------------------------|----------------------|-----------------------------|---------------------|------------------|------------------------|
| 1 | 0.00398 | 0.00394 | 1.01% | 250.9 | 253.81 | 1.16% |
| 10 | 0.000706 | 0.000329 | 53.40% | 1410 | 3003 | 112.98% |
| 100 | 0.000232 | 0.000166 | 28.45% | 4300 | 6002 | 39.58% |
| 1000 | 0.000236 | 0.000164 | 30.51% | 4220 | 6008 | 42.37% |

$$\text{Percent Error} = \frac{|\text{Actual} - \text{Expected}|}{\text{Expected}} * 100 \quad (1)$$

Explanation

The purpose of the lab was to test the limits of the ADC and the DAC using several different methods, the results of the experiment are shown in figures 1 through figures 15. Table 1 also shows the simulation and hardware results side by side to compare them. As the Table shows there seems to be a correlation to the increase in frequency and the percentage error between both the experiments. This could have been from many factors; the first factor is the difference in the blocks used from the hardware to the simulation. In the simulation, there were generic ADCs, DACs, resistors, and capacitors used which could lead to the higher percentage errors. At 1hz the percentage errors were only at 1.01% and 1.16% respectively between time steps and frequency.

The DAC did a better job reproducing frequencies at the lower end, as you can see the time steps in the 1hz 10hz and 100hz, in figures 2 through 15. The signals are better quality of the reconstruction seems to vary also as the frequency of the input signal increases. The resolution of a n-bit analog-to-digital Converter (ADC) is a function of how many parts the maximum signal can be divided into. The formula to calculate resolution is 2^n . For example, a 8 bit ADC has a resolution of $2^8 = 256$. Therefore, our best resolution is 1 part out of 256.[1] An ADC takes an analog signal and turns it into a binary number. Thus, each binary number from the ADC represents a certain voltage level. Resolution is the smallest input voltage change a digitizer can capture. Resolution can be expressed in bits (LSB), in proportions, or in percent of full scale. Resolution limits the precision of a measurement. The higher the resolution (number of bits), the more precise the measurement. An 8-bit ADC divides the vertical range of the input amplifier into 256 discrete levels. With a vertical range of 10 V, the 8-bit ADC cannot ideally resolve voltage differences smaller than 39 mV. In comparison, a 14-bit ADC with 16,384 discrete levels can ideally resolve voltage differences as small as 610 μ V. .[1]. In the system under test, this can be seen in the figures above how the bit resolution plays into the reconstruction of the signal and the step effect occurs.

There are some shortcomings to this design and any signal processing has its downsides. Here the resolution, device mechanics, and frequencies all play a role here. As in the voltage resolution the aliasing effect and so on, if the frequency increases too much the system cannot properly regenerate that signal. In all, the experiment was successful and the ADC and DAC were tested properly.

References

[1]N. Instruments, "Understanding resolution in high-speed Digitizers/Oscilloscopes," 2006.
[Online]. Available: <http://www.ni.com/white-paper/4806/en/>. Accessed: Jan. 27, 2017.

[2]N. Instruments, "Aliasing and sampling at frequencies above the Nyquist frequency," 2006.
[Online]. Available: <http://www.ni.com/white-paper/3000/en/>. Accessed: Jan. 27, 2017.