

## Lecture 9: Combinational Circuit Design


### Outline

- ☐ Bubble Pushing
- ☐ Compound Gates
- ☐ Logical Effort Example
- ☐ Input Ordering
- ☐ Asymmetric Gates
- ☐ Skewed Gates
- ☐ Best P/N ratio

## Example 1


```
module mux(input s, d0, d1,  
           output y);  
  
    assign y = s ? d1 : d0;  
endmodule
```

 1) Sketch a design using AND, OR, and NOT gates.









## Example 2

 2) Sketch a design using NAND, NOR, and NOT gates.  
Assume  $\sim S$  is available.



      
## Bubble Pushing

- ❑ Start with network of AND / OR gates
- ❑ Convert to NAND / NOR + inverters
- ❑ Push bubbles around to simplify logic
  - Remember DeMorgan's Law




## Example 3

 - 3) Sketch a design using one compound gate and one NOT gate. Assume  $\sim S$  is available.



# Compound Gates

## □ Logical Effort of compound gates

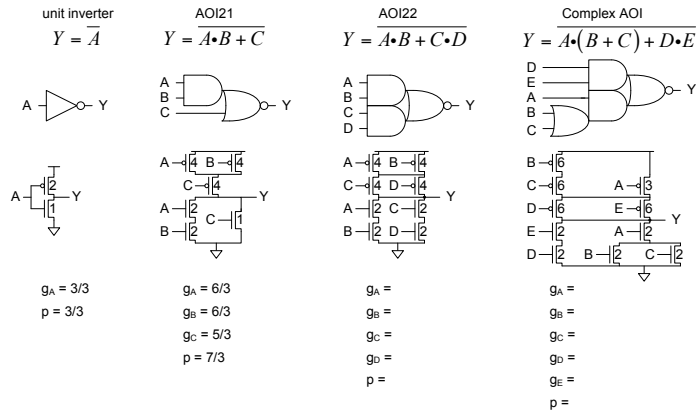

10: Combinational Circuits


CMOS VLSI Design 4th Ed.

7

## Example 4


- The multiplexer has a maximum input capacitance of 16 units on each input. It must drive a load of 160 units. Estimate the delay of the two designs.

H =

 

$P =$   
 $G =$   
 $F =$   
 $\hat{f} =$   
 $D =$

B = N =

 

$P =$   
 $G =$   
 $F =$   
 $\hat{f} =$   
 $D =$


10: Combinational Circuits

CMOS VLSI Design 4th Ed.

8

 
## Example 5

- Annotate your designs with transistor sizes that achieve this delay.



 
## Input Order

- Our parasitic delay model was too simple
  - Calculate parasitic delay for Y falling
    - If A arrives latest?
    - If B arrives latest?




 
## Inner & Outer Inputs

- ❑ Inner input is closest to output (A)
- ❑ Outer input is closest to rail (B)
- ❑ If input arrival time is known
  - Connect latest input to inner terminal



  
## Asymmetric Gates

- ❑ Asymmetric gates favor one input over another
- ❑ Ex: suppose input A of a NAND gate is most critical
  - Use smaller transistor on A (less capacitance)
  - Boost size of noncritical input
  - So total resistance is same
- ❑  $g_A =$
- ❑  $g_B =$
- ❑  $g_{\text{total}} = g_A + g_B =$
- ❑ Asymmetric gate approaches  $g = 1$  on critical input
- ❑ But total logical effort goes up




## Symmetric Gates

- Inputs can be made perfectly symmetric

 
 
## Skewed Gates

- Skewed gates favor one edge over another
- Ex: suppose rising output of inverter is most critical
  - Downsize noncritical nMOS transistor












- Calculate logical effort by comparing to unskewed inverter with same effective resistance on that edge.
  - $g_u =$
  - $g_d =$

## HI- and LO-Skew

- ❑ Def: Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition.
- ❑ Skewed gates reduce size of noncritical transistors
  - HI-skew gates favor rising output (small nMOS)
  - LO-skew gates favor falling output (small pMOS)
- ❑ Logical effort is smaller for favored direction
- ❑ But larger for the other direction



## Catalog of Skewed Gates

 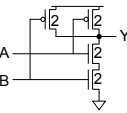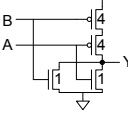 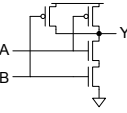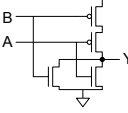 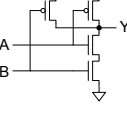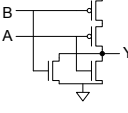	Inverter	NAND2	NOR2
unskewed	 $g_u = 1$ $g_d = 1$ $g_{avg} = 1$	 $g_u = 4/3$ $g_d = 4/3$ $g_{avg} = 4/3$	 $g_u = 5/3$ $g_d = 5/3$ $g_{avg} = 5/3$
HI-skew	 $g_u = 5/6$ $g_d = 5/3$ $g_{avg} = 5/4$	 $g_u =$ $g_d =$ $g_{avg} =$	 $g_u =$ $g_d =$ $g_{avg} =$
LO-skew	 $g_u = 4/3$ $g_d = 2/3$ $g_{avg} = 1$	 $g_u =$ $g_d =$ $g_{avg} =$	 $g_u =$ $g_d =$ $g_{avg} =$



  
## Asymmetric Skew

- ❑ Combine asymmetric and skewed gates
  - Downsize noncritical transistor on unimportant input
  - Reduces parasitic delay for critical input



 
## Best P/N Ratio

- ❑ We have selected P/N ratio for unit rise and fall resistance ( $\mu = 2-3$  for an inverter).
- ❑ Alternative: choose ratio for least average delay
- ❑ Ex: inverter
  - Delay driving identical inverter
  - $t_{pdf} =$
  - $t_{pdr} =$
  - $t_{pd} =$
  - $dt_{pd} / dP =$
  - Least delay for  $P =$


 
## P/N Ratios

- ❑ In general, best P/N ratio is sqrt of equal delay ratio.
  - Only improves average delay slightly for inverters
  - But significantly decreases area and power



## Observations

- ❑ For speed:
  - NAND vs. NOR
  - Many simple stages vs. fewer high fan-in stages
  - Latest-arriving input
- ❑ For area and power:
  - Many simple stages vs. fewer high fan-in stages