

ECES-303


Homework #2

From book: 7.12 and 7.30

Supplementary Problems:




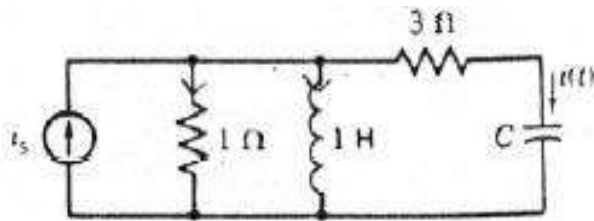- Find $I(t)$ for $t > 0$ using Laplace transform when $C = 1$ and $i_s e^t u(t)$ for the circuit of the following figure:




- A system with impulse response $h(t)$, has three poles located at $s = -3$, $s = 1 + 3j$ and $s = 1 - 3j$, and two zeros located at $s = 2 + j$ and $s = 2 - j$.
 - Write down an expression for $H(s)$.
 - If the system is BIBO stable find the region of convergence of $H(s)$.
 - Find $h(t)$.
- In the circuits shown, the switch is moved in accordance with the arrow at $t = 0$, having been in the top position for a long time. Solve for the current $I(t)$ for $t \geq 0$ using the Laplace transform.

(a)

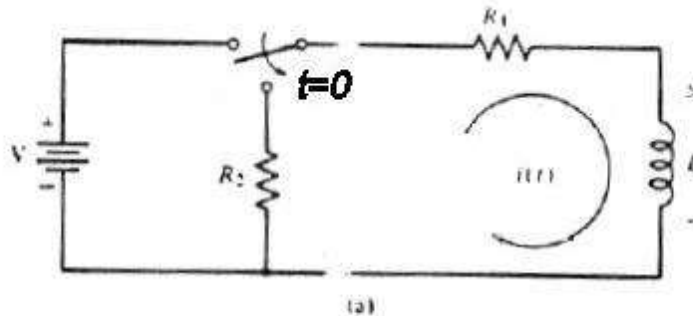

(b)

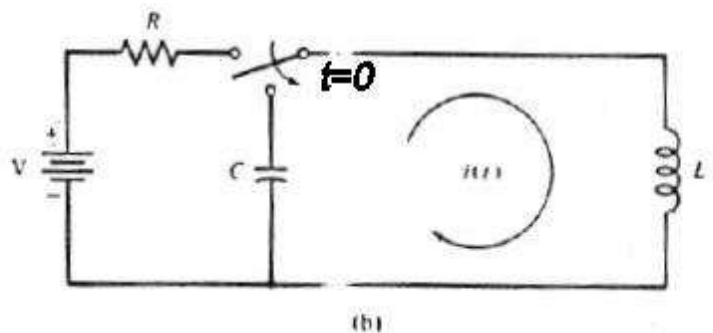

4. Using Laplace transforms, find the response $v(t)$ for $t > 0$ for the circuit of the following figure when $v_s = 6e^{3t} u(t)$ 