


Lecture 6: Logical Effort

Outline

- ☐ Logical Effort
- ☐ Delay in a Logic Gate
- ☐ Multistage Logic Networks
- ☐ Choosing the Best Number of Stages
- ☐ Example
- ☐ Summary


Introduction

- ❑ Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- ❑ Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

 

 Example

- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.
- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs $A[3:0]$
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?



Delay in a Logic Gate

- ❑ Express delays in process-independent unit $d = \frac{d_{abs}}{\tau}$
- ❑ Delay has two components: $d = f + p$
- ❑ f : effort delay = gh (a.k.a. stage effort)
 - Again has two components
- ❑ g : logical effort
 - Measures relative ability of gate to deliver current
 - $g = 1$ for inverter
- ❑ h : electrical effort = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout
- ❑ p : parasitic delay
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

$$\tau = 3RC$$

$\approx 3 \text{ ps in } 65 \text{ nm process}$
 $60 \text{ ps in } 0.6 \mu\text{m process}$

6: Logical Effort


CMOS VLSI Design 4th Ed.

5

Delay Plots

$$d = f + p$$

$$= gh + p$$

 


6: Logical Effort

CMOS VLSI Design 4th Ed.

6

Computing Logical Effort

 - ❑ DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- ❑ Measure from delay vs. fanout plots
- ❑ Or estimate by counting transistor widths



6: Logical Effort

CMOS VLSI Design 4th Ed.

7

Catalog of Gates

- ❑ Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

6: Logical Effort

CMOS VLSI Design 4th Ed.

8


Catalog of Gates

- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{osc} =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$

Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$


Multistage Logic Networks

- Logical effort generalizes to multistage networks

- Path Logical Effort* $G = \prod g_i$

- Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 - Path Effort* $F = \prod f_i = \prod g_i h_i$



Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$

❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$

❑ Can we write $F = GH$?

Paths that Branch

❑ No! Consider paths that branch:

$G =$


$H =$

$GH =$

$h_1 =$

$h_2 =$

$F =$

 

Branching Effort

❑ Introduce *branching effort*

- Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

❑ Now we compute the path effort

- $F = GBH$

Multistage Delays

❑ Path Effort Delay

$$D_F = \sum f_i$$

❑ Path Parasitic Delay

$$P = \sum p_i$$

❑ Path Delay

$$D = \sum d_i = D_F + P$$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is



- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B




6: Logical Effort

CMOS VLSI Design 4th Ed.

19

Example: 3-stage path

 

Logical Effort	$G =$
Electrical Effort	$H =$
Branching Effort	$B =$
Path Effort	$F =$
Best Stage Effort	$\hat{f} =$
Parasitic Delay	$P =$
Delay	$D =$

6: Logical Effort

CMOS VLSI Design 4th Ed.


20

Example: 3-stage path

- Work backward for sizes

y =

x =

 

6: Logical Effort


CMOS VLSI Design 4th Ed.

21

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

D =

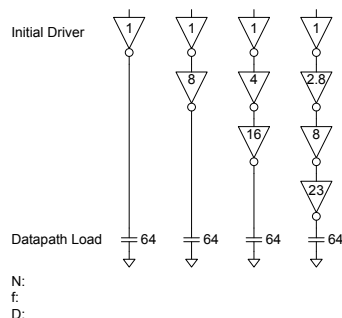

6: Logical Effort


CMOS VLSI Design 4th Ed.

22

Derivation

- ❑ Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- ❑ Define best stage effort $\rho = F^{\frac{1}{N}}$


$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Sensitivity Analysis

 
- ❑ How sensitive is delay to using exactly the best number of stages?



- ❑ $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy!
 - I like $\rho = 4$

 Example, Revisited

- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.



- ❑ Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs A[3:0]
 - Each input may drive 10 unit-sized transistors
- ❑ Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort: $H =$

Branching Effort: $B =$

- ❑ If we neglect logical effort (assume $G = 1$)

Path Effort: $F =$

Number of Stages: $N =$

- ❑ Try a -stage design

Gate Sizes & Delay

Logical Effort: $G =$


Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$

$y =$

 

Comparison

- ❑ Compare many alternatives with a spreadsheet
- ❑ $D = N(76.8 G)^{1/N} + P$

Design	N	G	P	D
NOR4	1	3	4	234
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

- | | |
|-----------------------------------|--|
| 1) Compute path effort | $F = GBH$ |
| 2) Estimate best number of stages | $N = \log_4 F$ |
| 3) Sketch path with N stages | |
| 4) Estimate least delay | $D = NF^{\frac{1}{N}} + P$ |
| 5) Determine best stage effort | $\hat{f} = F^{\frac{1}{N}}$ |
| 6) Find gate sizes | $C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$ |

Limits of Logical Effort

- ☐ Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- ☐ Simplistic delay model
 - Neglects input rise time effects
- ☐ Interconnect
 - Iteration required in designs with wire
- ☐ Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- ❑ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- ❑ Provides language for discussing fast circuits
 - But requires practice to master