

ECEL 304

LECTURE 1

This course offers laboratory experience, using both modeling software and digital and analog hardware relevant to both electrical and computer engineers.

PERSONNEL



**Taif
Choudhury**

**Bossone 216
215-895-6857
tai@coe.drexel.edu**

**Office Hours:
Tues., 5 PM – 6 PM**



**Jesse
Hill**

**Bossone 414
jrh62@drexel.edu**

**Office Hours:
BY APPOINTMENT
ONLY**

**Zhihuan
Wang**

**Bossone 515
zw78@drexel.edu**

**Office Hours:
BY APPOINTMENT
ONLY**



**Dominic
Imbrenda**

**Bossone 324
di22@drexel.edu**

**Office Hours:
BY APPOINTMENT
ONLY**



COURSE DESCRIPTION

- **Build an audio recorder**
 - 10 week design project (entire term)
 - Record from mic, playback through speaker
 - ADC, DAC and RAM
 - Counters, Timers, Gates, Flip-flops, etc.
- **Practical experience with circuit building and design**
 - Design aspect will be stressed
- **Circuit simulations done in Multisim**
 - Very Similar to OrCAD Cadence

COURSE OPERATION

- **1 Hour Lecture in Nesbitt 111**
 - Lecture will be recorded and posted within a day
 - No electronic devices (phones, laptops, etc.)
- **2 Hour Lab in Bossone 205**
 - No open toed-shoes
 - Come to lab prepared
- **Primarily rely on BBLearn**
 - Currently in progress of getting it up...
 - All communication/announcements
 - Lab report submissions
 - Grade distribution
 - Lecture videos
 - Make sure you enable email notifications

EXPECTATIONS

- Attendance is mandatory!
 - Work in groups of 2 (same group entire term)
 - Equal work between all group members
- At LEAST 4-6 Hours of work outside of lab
- Assignments turned in on time
 - Late policy explained later
- Academic honesty
 - See Drexel's policy on this:
http://www.drexel.edu/provost/policies/academic_dishonesty.asp
 - WILL FOLLOW VERY STRICTLY

GRADING

Attendance	5%
Quizzes	20%
Worksheets	20%
Reports	20%
Initial Project Checkoff	15%
Final Project Checkoff	20%
Extra Credit #1	5%
Extra Credit #2	5%

ATTENDANCE

- Attendance is **MANDATORY**
 - For both Lecture AND Lab
- Lecture Attendance (5%)
 - Use Dragoncard to sign-in
 - Your responsibility to make sure you sign in
- Lab Attendance
 - Determined by worksheet checkoff
 - Report will NOT be accepted if absent

QUIZZES (20%)

- Each quiz is 10 Points and 10 Minutes Long
- Will be given at the very beginning of lab
- NO make-up quizzes will be given
 - Unless you have a doctor's note, funeral, etc.
 - Do NOT miss a lab
 - Do NOT show up late to lab
- Will cover material from previous weeks
 - Pay attention during lecture AND lab
- Format will vary
 - Multiple Choice, Short Answer, True/False, etc.
- Announced ahead of time
 - During lecture and/or through BBLearn

WORKSHEET (20%)

- **Each worth 10 Points**
- **Group assignment (1 worksheet/group)**
 - Cannot work outside of your group
 - Same grade for all individuals in the group
- **To be checked off by the end of lab**
 - Will NOT be accepted after lab is over
 - Will be at the complete discretion of your TA
 - Your responsibility to get it checked off
- **Keep worksheet after it is checked off**
 - Use as reference to write your lab report
 - Do NOT just copy & paste from your worksheet
 - Do NOT submit your worksheet with your report

PROJ. CHECKOFF (35%)

- **Initial Project Checkoff (15%)**
 - Ensure you are on track and nearly complete
 - Successfully recording from Function Generator
 - Successfully playing back on Oscilloscope
- **Final Project Checkoff (20%)**
 - Fully completed AND functional audio recorder
 - Successfully recording from microphone
 - Successfully playing back on speaker
- **Rubric used for each project checkoff**
 - Will be based on your projects design, quality and performance

EXTRA CREDIT (10%)

- **Extra Credit #1 (5%)**
 - Implement additional functionality to recording/playback that wasn't covered
 - Including but not limited to: advanced filtering, bass boost, automatic gain control, etc.
- **Extra Credit #2 (5%)**
 - Use microcontroller to replace external circuitry
 - Control logic, amplifier, maybe even RAM?
- **Partial credit given**
 - Depends on complexity and completeness
- **May do either one, both or neither**
- **More details to follow...**

REPORTS (20%)

- **100 Points**
- **Individually written reports**
 - See “Academic Honesty Policy” in syllabus
- **Due Friday by 11:59 PM (BEFORE MIDNIGHT)**
 - Friday of the next calendar week the lab was performed
 - Submit via BBLearn (Do NOT email it)
 - 3% penalty per day late
 - Not accepted after 4 weeks

REPORT FORMAT

- **Cover Page (5%)**
 - Use the one provided on BBLearn!
- **Objective (10%)**
 - State what you're trying to accomplish/purpose
 - Very concise summary of what you did
 - DO NOT paraphrase the lab procedure
 - Some background info (provide reference if required, cite properly)
 - 1 - 2 paragraphs long

REPORT FORMAT

- **Results (35%)**
 - **Tables**
 - Manual voltage sweep, resistor tolerances, etc.
 - **Graphs (Any and all collected)**
 - Multisim output, oscilloscope screen capture, etc.
 - **Equations**
 - **Correctly labeled**
 - **Elaborate where appropriate**

REPORT FORMAT

- **Explanation (50%)**
 - 1 – 2 pages long
 - Discusses and explains your results (reference your graphs, tables and equations)
 - Compare theoretical, simulated and experimental
 - Answer any/all questions in lab procedure
 - Discussion of errors AND sources of error
 - Example:
 - “We calculated the theoretical voltage to be 3.53 V (Equation 2) but the experimental design yielded 3.49 V (Table 6), an error of 1.13% (Table 7). This is attributable to the tolerance of the resistor (Table 5) being...”
 - Make a conclusion, did you achieve your objective?

REPORT FORMAT

- **References**
 - Optional, but you MUST provide this if you used an outside source
 - MUST use IEEE format
- **Appendix**
 - Also optional
 - Include only if you have data that isn't required but feel should be included
 - Calculations, figures, tables, etc..

REPORT STRUCTURE

- **FOLLOW GIVEN FORMAT!!!**
- **General guidelines apply**
 - Page numbering, labeling equations, figures and tables appropriately (IEEE formatting)
 - Points WILL be taken off for incorrect spelling/grammar/formatting
- **Use worksheet as a guide to help you**
 - Do NOT copy and paste from worksheet
- **See “Lab Report Structure Guide”**

REPORT RECAP

- **Cover Page (5%)**
- **Objective (10%)**
- **Results (35%)**
- **Explanation (50%)**
- **References (Optional)**
- **Appendix (Optional)**


Worth 20% of your final grade

QUESTIONS?



PROJECT OVERVIEW


Eventually try to achieve this:

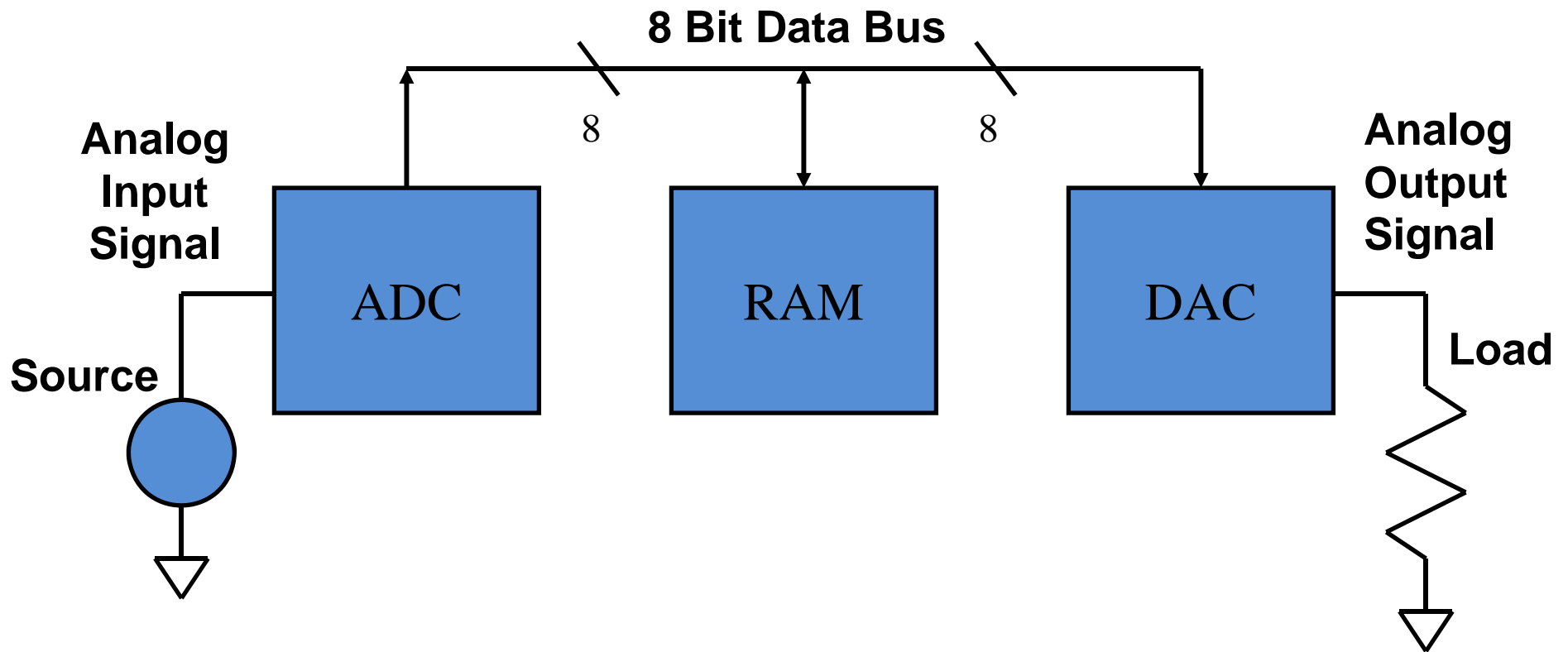

- ANALOG INPUT goes into ADC, converts to DIGITAL
- DIGITAL goes into DAC converts back to ANALOG
- DIGITAL goes/comes out of the RAM

DATA/BUS CONTENTION



DATA CONTENTION
HERE

 

- Two simultaneous outputs
 - Outputs “fight” to assert value on line
 - Leads to ambiguous or unknown data
 - Could damage hardware
 - **AVOID AT ALL COSTS!!!**


DATA/BUS CONTENTION

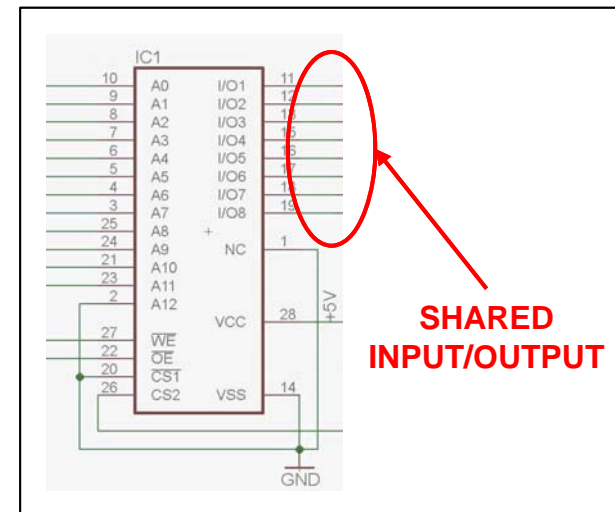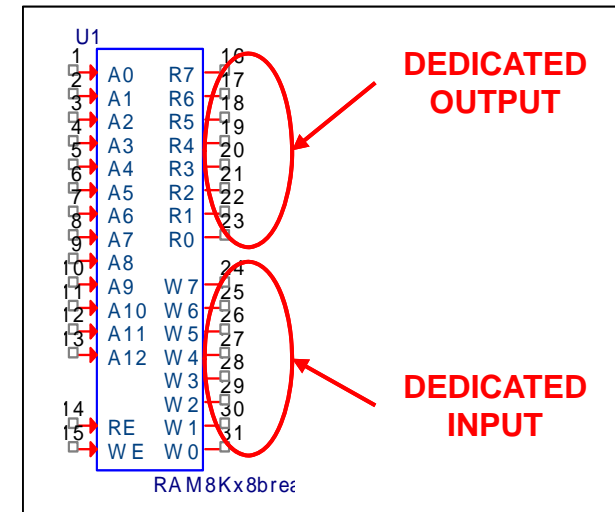- Problem arises because of the RAM
- Most RAMS use the same lines for INPUTS AND OUTPUTS
 - MUST switch between READ or WRITE
 - Can either READ or WRITE to RAM at a time
 - CANNOT do BOTH simultaneously




CONTENTION SOLUTION

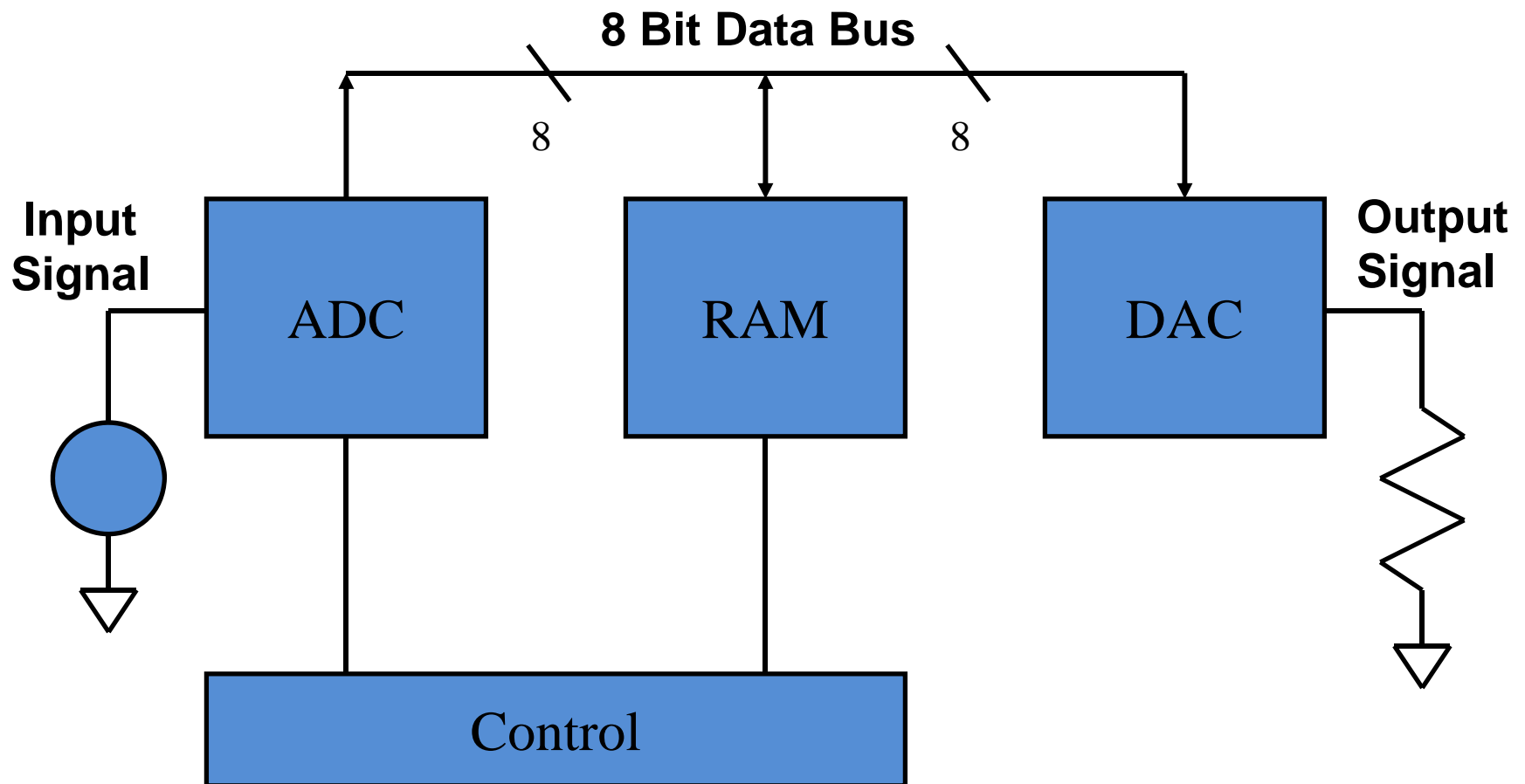
- Add Control Circuitry to the system
- ADC MUST have control pins



RECORDING PHASE

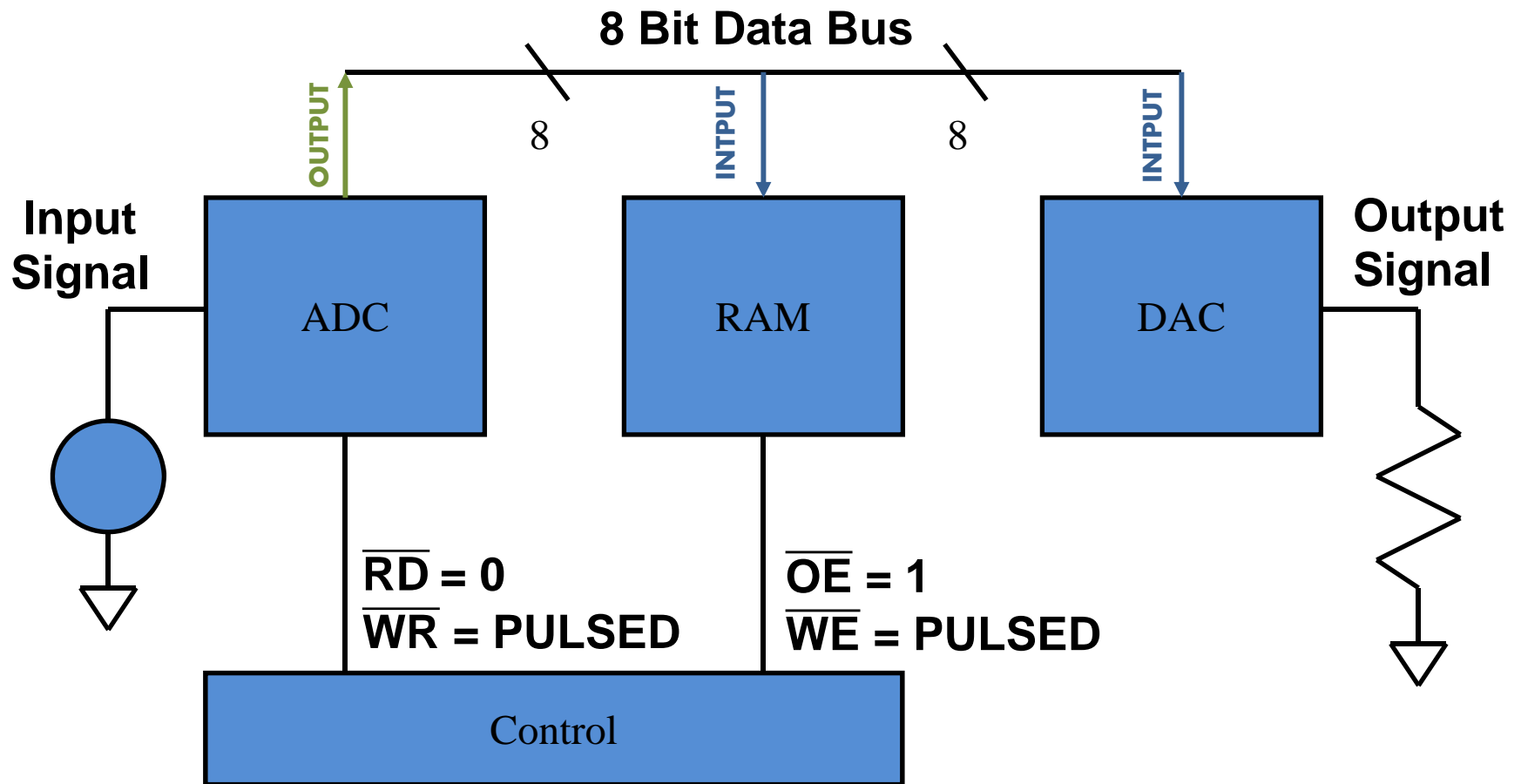


PLAYBACK PHASE

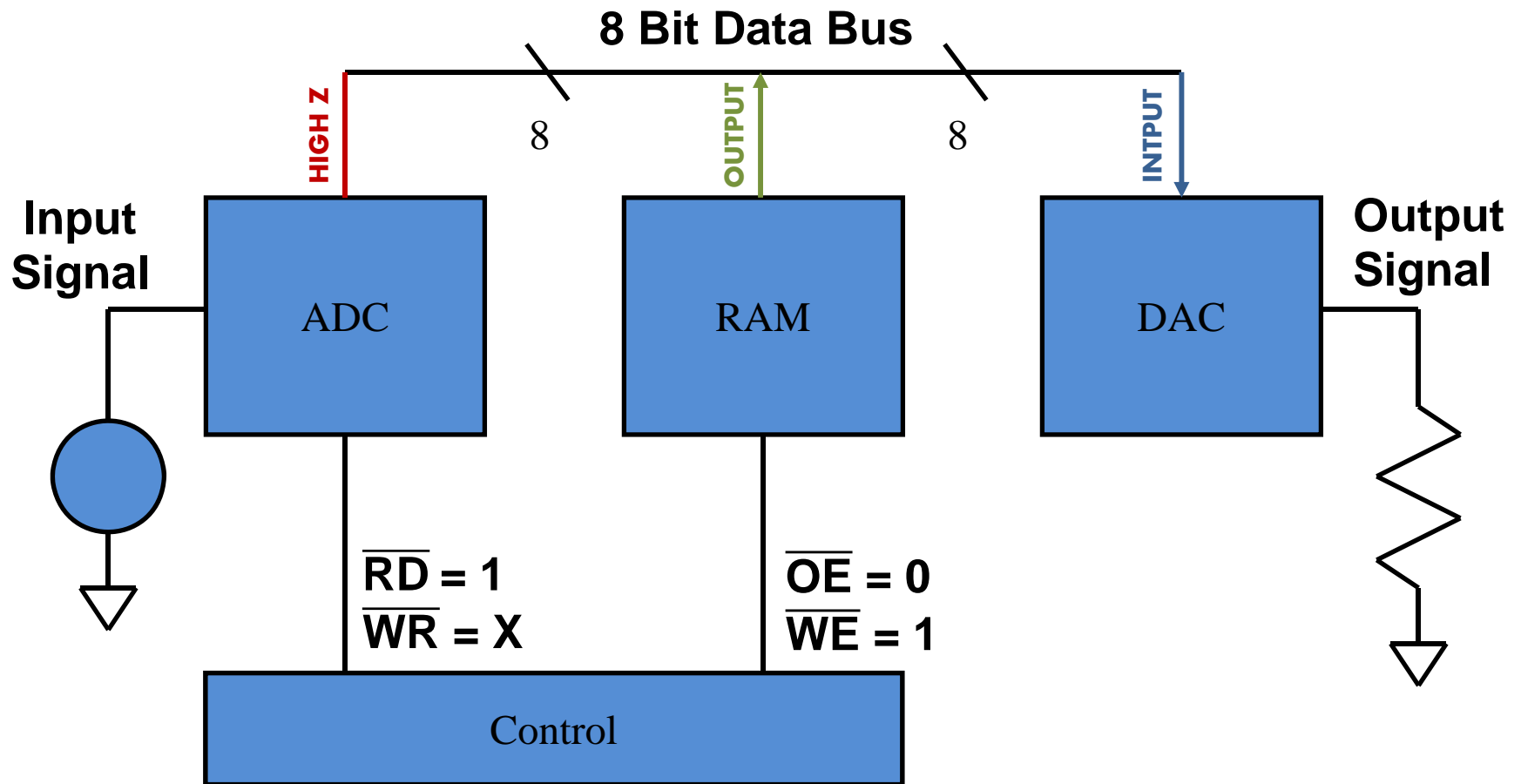

NOTE: ADC is put into HIGH Z state, ADC output is disabled

LAB OVERVIEW

For this week, we'll do the following:

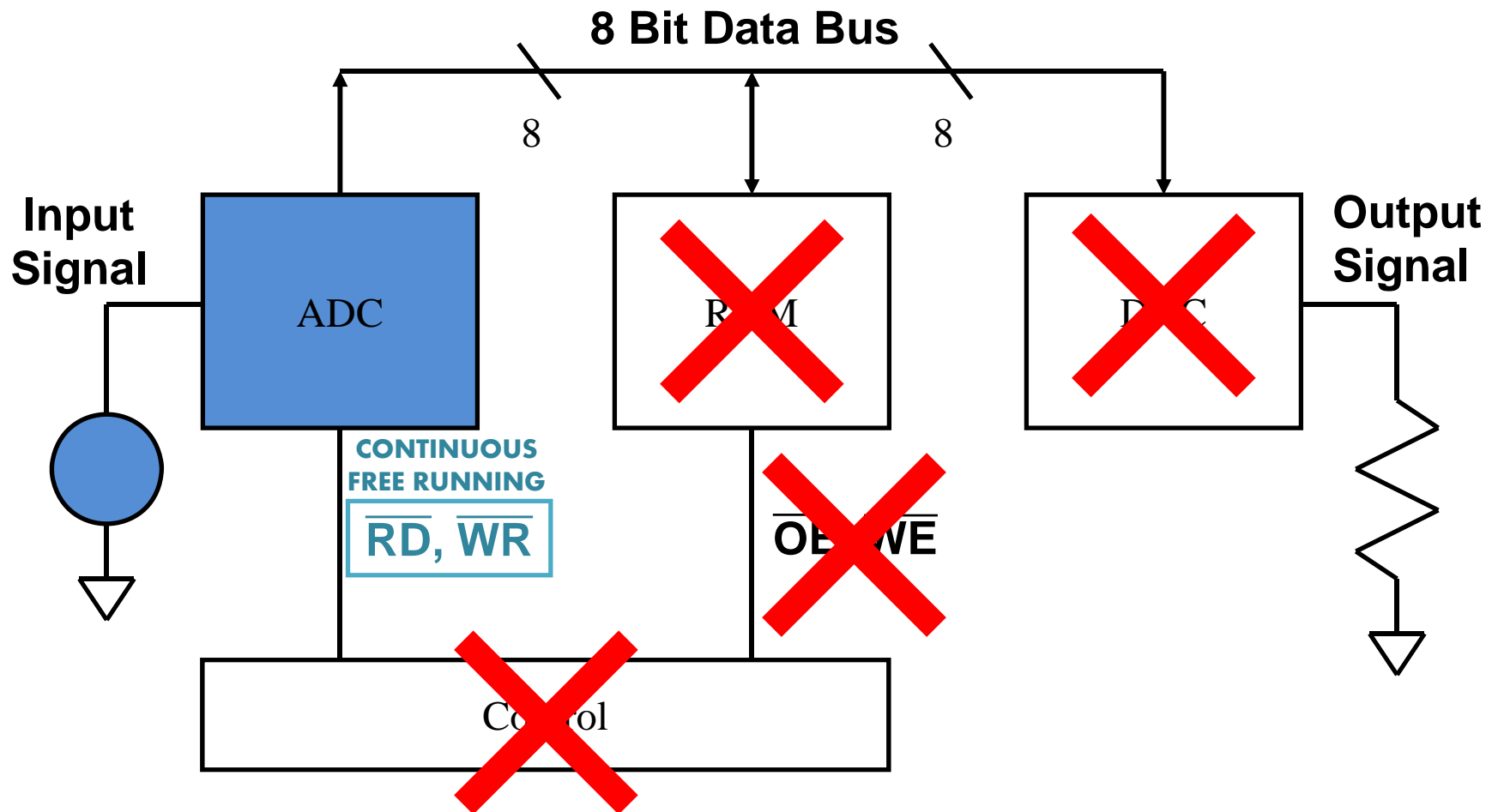


ADC REINTRODUCED

- **ADC (Analog to Digital Converter)**
 - Should be familiar from ECEL 303
 - Converts a given voltage input into digital bits
 - Number of digital bits or outputs vary depending on the ADC
- **Will be using the ADC 0804**
 - 8 bit output
 - Capable of self-clocking
 - Can disable output (Put in High Impedance)
- **Will test on ECEL 304 Board this week**


SUC. APPROX. ADC

- **Successive Approximation ADC**
 - This design requires only a single comparator and will be only as good as the DAC used in the circuit.
 - The analog output of a high-speed DAC is compared against the analog input signal.
 - The digital result of the comparison is used to control the contents of a digital buffer that both drives the DAC and provides the digital output word.


SUC. APPROX. ADC

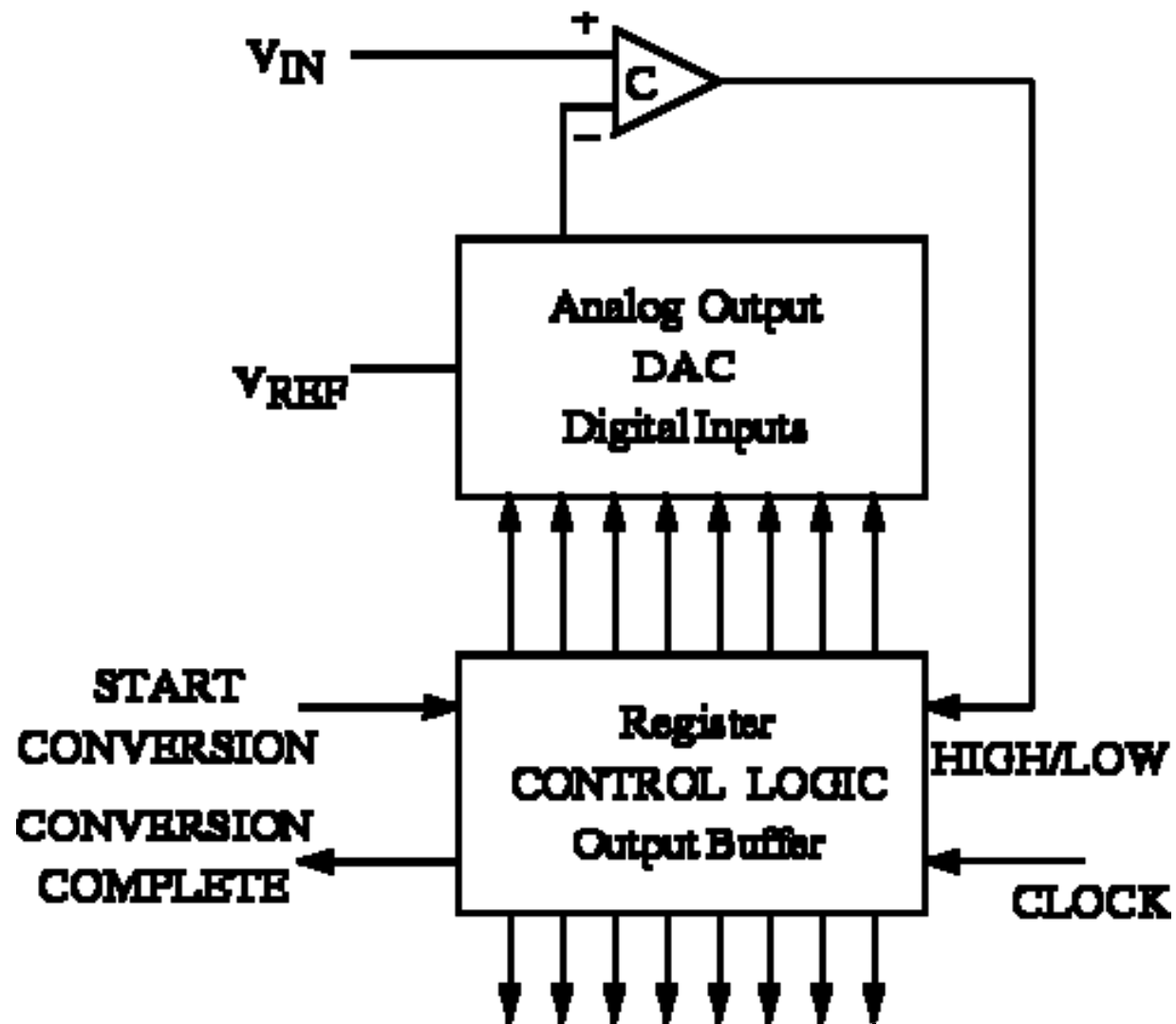

INSIDE THE ADC 0804

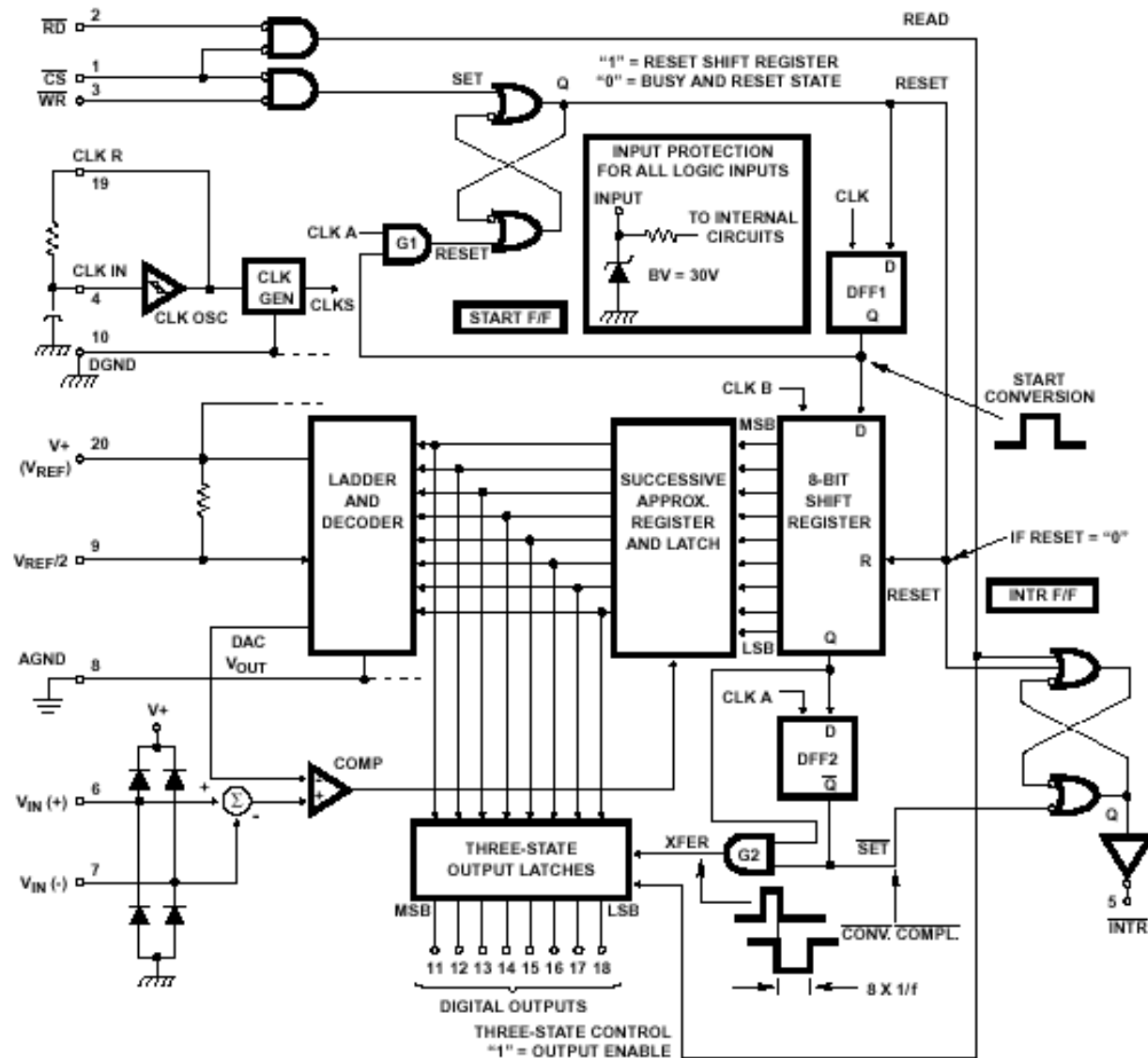

ADC 0804 SCHEMATIC

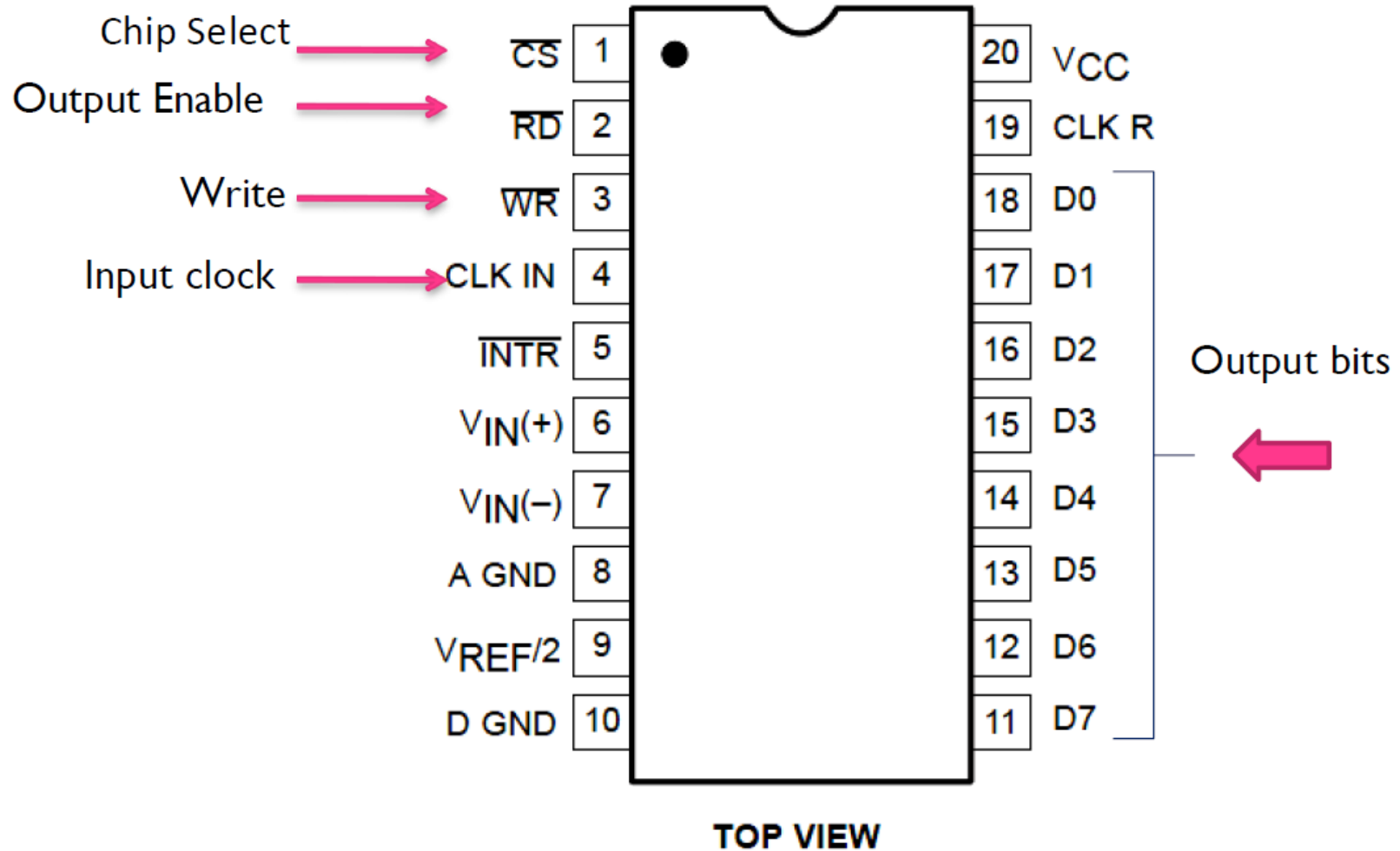

ADC OPERATION

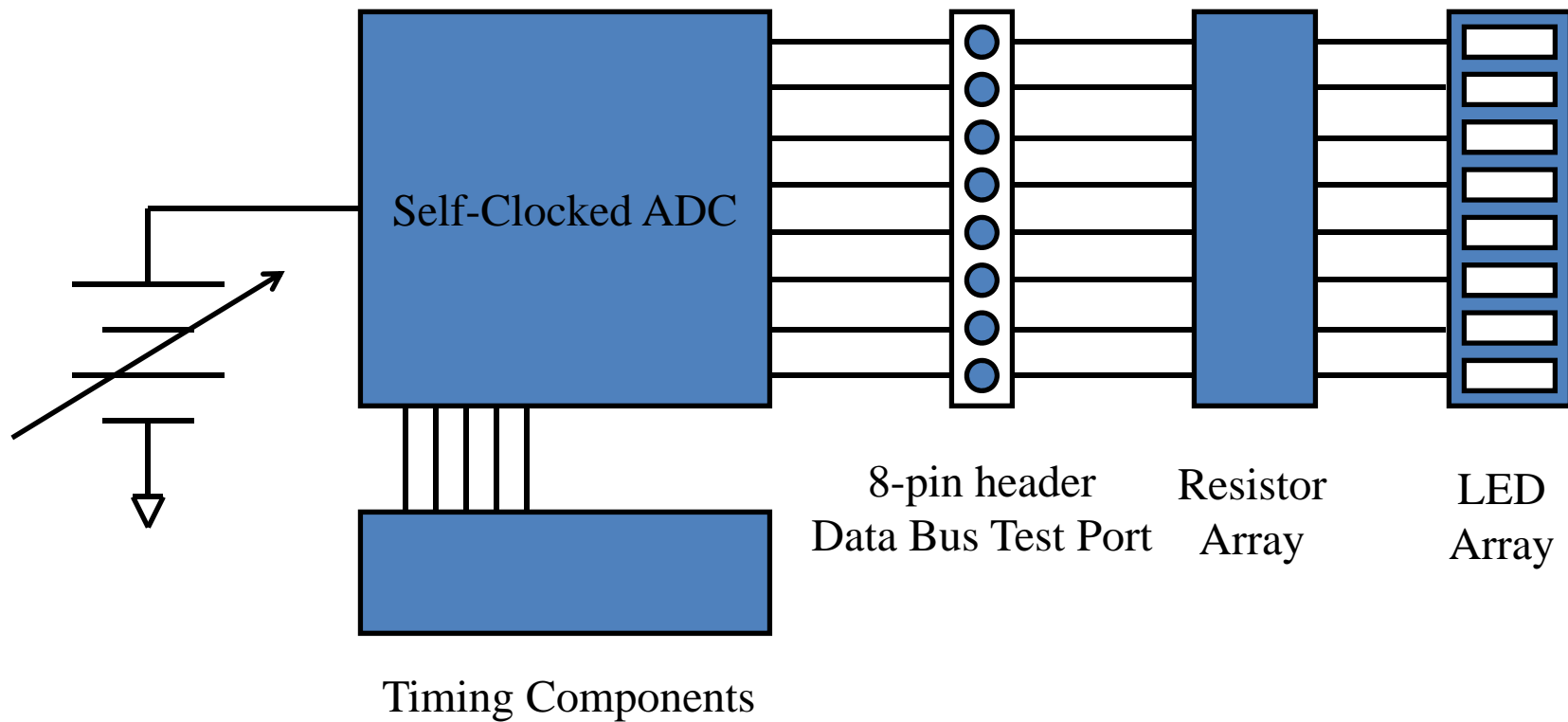


Figure 17/18, ADC0804 data sheet

SELF CLOCKED MODE

- **All synchronous digital IC requires a clock signal**
 - **Allows control over different components used in circuit**
 - **Keeps components running at same speed or synchronized**
 - **Components normally operate on either rising or falling edge of clock signal**
- **ADC 0804 has an internal clock generator**
 - **Does not need external clock**
 - **Set by a single timing resistor and capacitor**


CLOCK MODES

EXTERNAL CLOCKING

- An external clock is applied to the clock input of the convertor, pin 4

INTERNAL OR SELF CLOCKING COMPARATOR WITH HYSTERESIS

 - Pin 19 is connected to pin 4, the input clock signal
- Clock frequency can be controlled by R and C




$$f = \frac{1}{1.1RC}$$

ADC 0804 SIGNALS

- Remember, signals with a bar on top are ACTIVE LOW
 - Normally High or 1
- Signals (**BLUE – OUTPUT**, **GREEN - INPUT**):
 - \overline{WR} - Rising edge of signal starts sampling
 - \overline{RD} - Enables/disables the output
 - \overline{INTR} - Pulses low when done sampling
 - \overline{CS} - Chip select, always goes to ground
 - **GND** - Ground
 - **VCC** - Power, usually +5 V

TIMING DIAGRAM

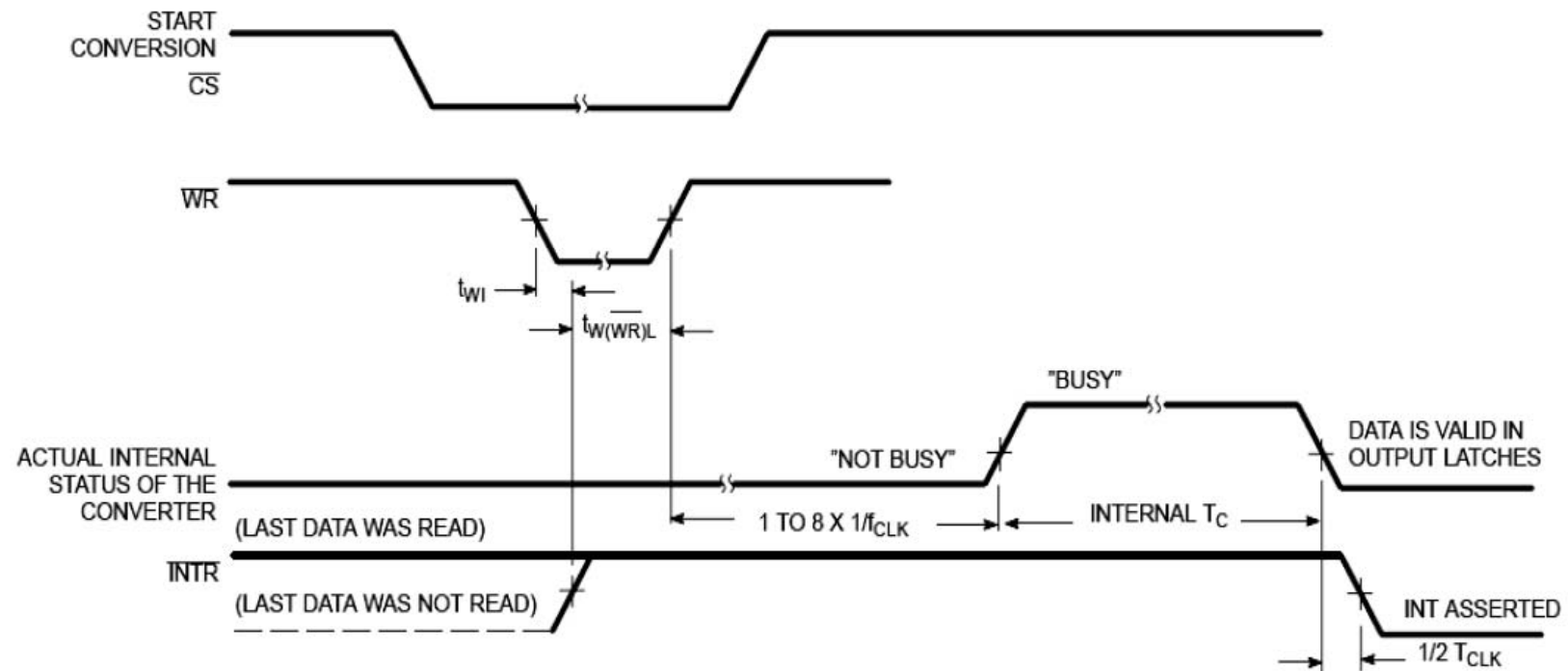

T_c is 64 clock cycles, total ADC
conversion time is about 73 clock cycles

CONT. FREE RUNNING

- ADC will be operated in Continuous Free-Running Mode
 - Continuous - Immediately starts sampling again after last sample is determined
 - Free-Running - No external circuitry required to make it operate
 - In other words, in this mode, the ADC continuously samples the input without any external trigger

FREE RUNNING MODE

 


FIGURE 18. BASIC TESTER FOR THE A/D

CALCULATING FREQ

 


FIGURE 5. f_{CLK} vs CLOCK CAPACITOR


$$f_{CLK} = \frac{1}{1.1RC}$$

$$f_S = \frac{f_{CLK}}{CCPS}$$

$CCPS$:
Clock Cycles
Per Sample

INTR IN CFR MODE

 $T_c = \text{clock cycle or period}$
 $f_c = \text{clock frequency}$



Sampling Frequency $f_s = \frac{1}{T_s}$

$\frac{f_c}{f_s} = \frac{T_s}{T_c} = \# \text{ of clock cycles required for one conversion}$

BINARY TO DECIMAL

- **Use Base-2 Radix Formula:**

$$N = 2^n B_n + 2^{n-1} B_{n-1} + \dots + 2^1 B_1 + 2^0 B_0$$

- **Example: Convert 1001 into decimal**

$$N = 2^3(1) + 2^2(0) + 2^1(0) + 2^0(1) = \\ 2^3 + 2^0 = 8 + 1 = 9$$

- **BE CAREFUL WHEN CALCULATING FOR ADC!!!**
 - LEDs are active LOW!!!
 - MUST invert (flip) bits first

VOLTAGE CALCULATION

- Your ADC will output 8 bits, which can be grouped as 4 high (MS – Most Significant) and 4 low (LS – Least Significant) bits
- The voltage represented by the digital output is given by:

$$V_{out} = \left(\frac{MS}{16} + \frac{LS}{256} \right) V_{ref}$$


LAB OVERVIEW

- **Design and build ADC circuit**
 - Pick timing resistor and capacitor
 - Some additional wiring
- **Change DC input voltage and record output**
 - Verify accuracy
 - Determine ADC voltage resolution
- **Apply analog voltage**
 - Measure output using logic analyzer
 - Using a ramp input, observe binary count
 - Observe operation of ADC internal clock
- **Simulate the all hardware steps in Multisim**


DESIGN CONSIDERATION

- **What is the bandwidth of human speech?**
 - Provide a reference in your report
- **At what frequency should I sample?**
 - Higher frequency
 - Higher quality
 - Short recording/playback time
 - Lower frequency
 - Lower quality
 - Longer recording/playback time
- **Provide clear justification for your choice**
- **Performance limitations of this ADC chip?**
 - **READ THE DATASHEET!!!**


DATA ACQ. BOARD

 


SOCKETS

 

HEADERS/TERMINALS

 

CONTROL SIGNALS

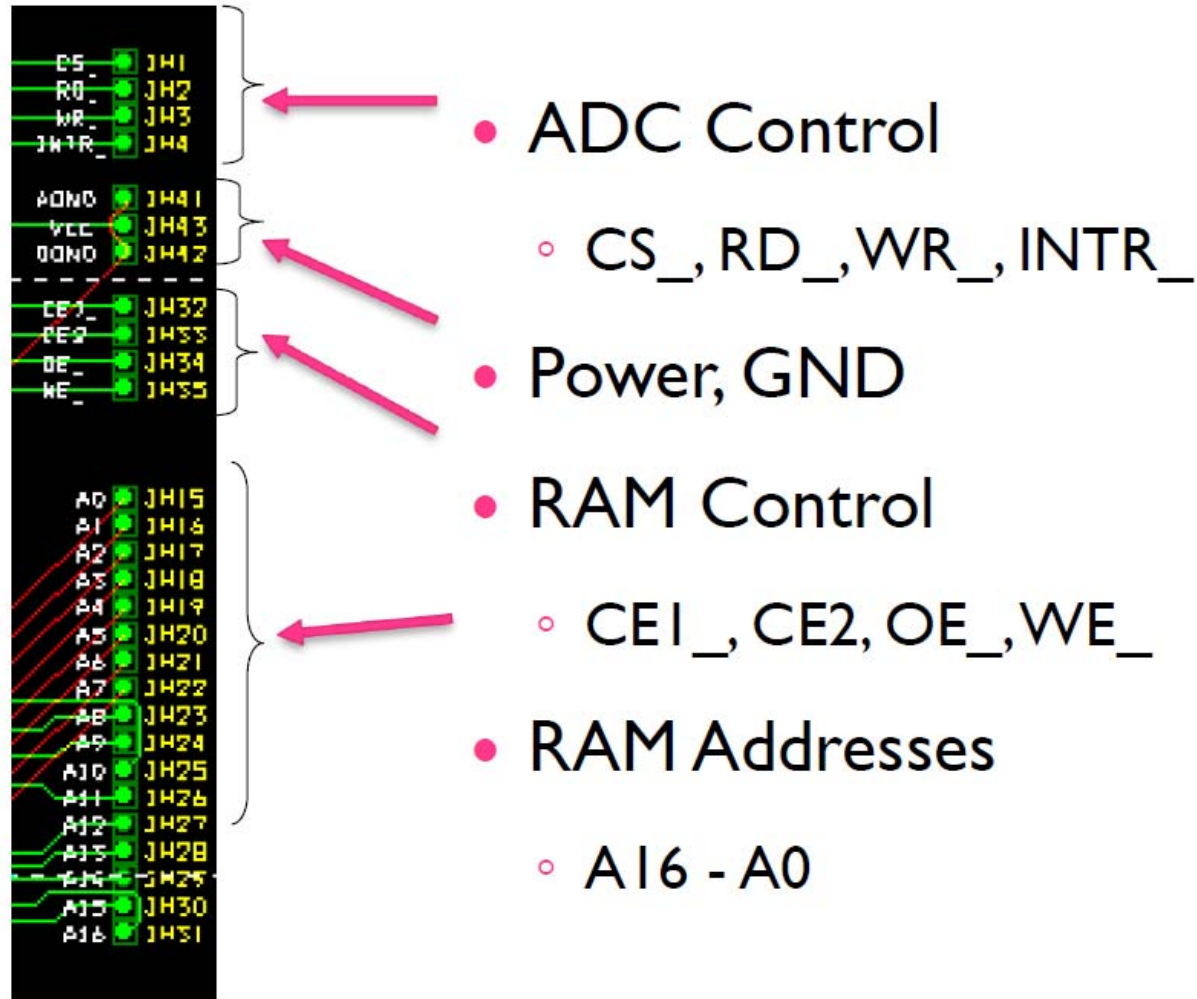


LAYOUT CONCERNS

- **Place chips that interact with each other nearby**
 - Less delay
- **Wire Length makes a difference**
 - Shorter Wires – Less Resistance/Capacitance
 - Longer Wires – More Resistance/Capacitance
- **Keep Analog Circuitry away from Digital Circuitry**
 - Potential problems with “crosstalk” – wireless interference between close signals

LOGIC ANALYZER

Use *Intuilink* to capture data

 

Analog and
digital
displays

Digital Menu
Access Button

Digital Menu
Access Button

LOGIC ANALYZER

- **There is an HP mixed-signal scope in each rack in Bossone 205**
- **The digital portion of the scope (logic analyzer) serves the same purpose as the LEDs, but it can do it at a higher speed**
- **To capture data, you need to capture screenshots from the Intuilink software on the lab computer**
- **Be sure to capture and save all data/screens**

PREPARING FOR LAB

- **Make sure to read over the instructions before the lab**
 - Will make some changes to it (clear up some instructions)
- **Familiarize yourself with Multisim**
 - Watch videos posted on BBLearn
- **Go over ADC 0804 Lab from ECEL 303**
 - Also posted on BBLearn
- **Watch video on using the Logic Analyzer**
 - To be posted later today...

NEXT WEEK

- **No in-class lecture next week**
 - **MLK day, University Holiday**
- **Lecture video will be posted on BBLearn**
 - **Expect it posted by Monday evening**
 - **Must watch before MIDNIGHT, Tuesday, Jan. 17**
 - **Will count towards lecture attendance**
- **Quiz next week during Lab**
 - **On the lecture/lab content from this week**
 - **Message will be sent out outlining content**

QUESTIONS?

